



(PART TWO – 10 Marks for each question)

Solution

Answer all the following questions

Q1)

Set up a midpoint Self bias for N-channel JFET with $I_{DSS} = 14 \text{ mA}$ and $V_{GS(off)} = -10 \text{ V}$. Use a 24 V dc source as the supply voltage. Show the circuit and resistor values. Indicate the values of I_D , V_{GS} , and V_{DS} .

Solution

$$I_D = \frac{I_{DSS}}{2} = \frac{14 \text{ mA}}{2} = 7 \text{ mA}$$


$$V_{GS} = \frac{V_{GS(off)}}{3.414} = \frac{-10 \text{ V}}{3.414} = -2.93 \text{ V}$$

Since $V_G = 0 \text{ V}$, $V_S = V_G$.

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{2.93 \text{ V}}{7 \text{ mA}} = 419 \Omega \text{ (The nearest standard value is } 430 \Omega \text{.)}$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{24 \text{ V} - 12 \text{ V}}{7 \text{ mA}} = 1.7 \text{ k}\Omega \text{ (The nearest standard value is } 1.8 \text{ k}\Omega \text{.)}$$

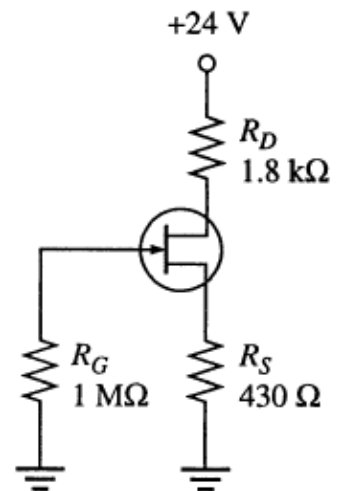Select $R_G = 1.0 \text{ M}\Omega$. See Figure



Q2)

What is the total output voltage for the loaded amplifier in Figure 1? $I_{DSS} = 8 \text{ mA}$; $V_{GS(off)} = -7 \text{ V}$; $V_{in} = 50 \text{ mV rms}$.

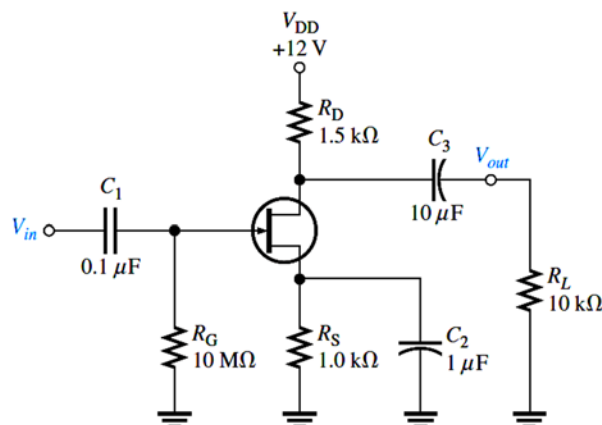


Figure 1.

Solution

Using mathematical approach we find:

يمكنك اثبات المعادلات الآتية الخاصة بـ (A, B, C) او استخدامها مباشرة بدون اثباتها

$$\begin{aligned} I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = I_{DSS} \left(1 - \left| \frac{I_D R_S}{V_{GS(off)}} \right| \right)^2 \\ &= I_{DSS} \left(1 - \frac{2I_D R_S}{|V_{GS(off)}|} + \left(\frac{I_D R_S}{|V_{GS(off)}|} \right)^2 \right) \\ I_D &= I_{DSS} - \frac{2I_{DSS} R_S}{|V_{GS(off)}|} I_D + \frac{I_{DSS} R_S^2}{V_{GS(off)}^2} I_D^2 \end{aligned}$$

Rearranging into a standard quadratic equation form,

$$\left(\frac{I_{DSS} R_S^2}{V_{GS(off)}^2} \right) I_D^2 - \left(1 + \frac{2I_{DSS} R_S}{|V_{GS(off)}|} \right) I_D + I_{DSS} = 0$$

The coefficients and constant are, $AI_D^2 + BI_D + C = 0$

$$A = \left(\frac{I_{DSS} R_S^2}{V_{GS(off)}^2} \right)$$

$$B = - \left(1 + \frac{2I_{DSS} R_S}{|V_{GS(off)}|} \right)$$

$$C = I_{DSS}$$

$$I_{D1,2} = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$A = \left(\frac{I_{DSS} R_S^2}{V_{GS(off)}^2} \right) = \frac{8 \times 10^{-3} \times 1000^2}{(7)^2} = 163.265$$

$$B = - \left(1 + \frac{2I_{DSS} R_S}{|V_{GS(off)}|} \right)$$

$$B = - \left(1 + \frac{2 \times 8 \times 10^{-3} \times 1000}{|-7|} \right) = -3.286$$

$$C = I_{DSS} = 8 \times 10^{-3}$$

$$I_{D1,2} = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$= \frac{3.286 \pm \sqrt{(-3.286)^2 - 4 \times 163.265 \times 8 \times 10^{-3}}}{2 \times 163.265}$$

$$I_{D1} = \frac{3.286 + \sqrt{5.571}}{326.53} = 17.292 \text{ mA}$$

$$I_{D2} = \frac{3.286 - \sqrt{5.571}}{326.53} = 2.835 \text{ mA}$$

We have two different solutions; we must choose the I_D value less than I_{DSS} . (Or, we must choose the value of I_D that makes $|V_{GS}| < |V_{GS(off)}|$).

$$I_D = 2.835 \text{ mA}$$

Using this value, calculate V_D .

$$V_D = V_{DD} - I_D R_D = 12 \text{ V} - (2.835 \text{ mA})(1.5 \text{ k}\Omega) = 7.75 \text{ V}$$

Next calculate g_m as follows:

$$V_{GS} = -I_D R_S = -(2.835 \text{ mA})(1000 \Omega) = -2.835 \text{ V}$$

$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|} = \frac{2 \times 8 \times 10^{-3}}{7} = 2.286 \text{ mS}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right) = 2.286 \text{ mS} \left(1 - \frac{-2.835}{-7} \right) = 1.36 \text{ mS}$$

Finally, find the ac output voltage.

$$V_{out} = A_v V_{in} = (g_m R_D // R_L) V_{in} = 1.36 \text{ mS} \times \frac{1.5 \text{ k}\Omega \times 10 \text{ k}\Omega}{1.5 \text{ k}\Omega + 10 \text{ k}\Omega} \times 50 \text{ mV}$$

$$V_{out} = 88.69 \text{ mV rms} \cong 89 \text{ mV rms}$$

Q3)

For the unloaded E-MOSFET amplifier in Figure 2, if $I_{D(on)} = 8 \text{ mA}$ at $V_{GS} = 12 \text{ V}$, $V_{GS(th)} = 4 \text{ V}$, and $g_m = 4500 \mu\text{S}$. Find V_{GS} , I_D , V_{DS} , and the rms output voltage V_{ds} .

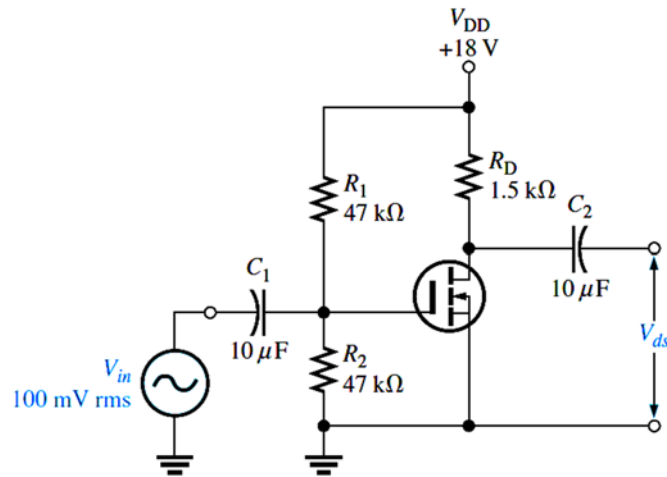


Figure 2.

Solution

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{47 \text{ k}\Omega}{94 \text{ k}\Omega} \right) 18 \text{ V} = \mathbf{9 \text{ V}}$$

$$K = \frac{I_{D(\text{on})}}{(V_{GS} - V_{GS(\text{th})})^2} = \frac{8 \text{ mA}}{(12 \text{ V} - 4 \text{ V})^2} = 0.125 \text{ mA/V}^2$$

$$I_D = K(V_{GS} - V_{GS(\text{th})})^2 = 0.125 \text{ mA/V}^2 (9 \text{ V} - 4 \text{ V})^2 = \mathbf{3.13 \text{ mA}}$$

$$V_{DS} = V_{DD} - I_D R_D = 18 \text{ V} - (3.125 \text{ mA})(1.5 \text{ k}\Omega) = \mathbf{13.3 \text{ V}}$$

$$A_v = g_m R_D = 4500 \text{ }\mu\text{S}(1.5 \text{ k}\Omega) = 6.75$$

$$V_{ds} = A_v V_{in} = 6.75(100 \text{ mV}) = \mathbf{675 \text{ mV rms}}$$